

**CSE 3203 CT 4 Assignment**  
**Roll No: 1903179**

**Assignment :** *Built a CPU based on following requirements:*

1. Word Size of CPU = 3
2. ALU Operations = ADD, ROL, OR
3. Register Number = 5
4. Size of RAM = 7
5. Word size of ISA and RAM = 16
6. CPU Instructions = Branching(JC, JMP), Reg, Imm

**Solution:**

**Video Link (Youtube Video Link):** <https://youtu.be/Rh-h33NvQTE>


In the first 7 clock cycle, instructions from ROM were copied to RAM. Then the PCenable pin was turned to 1 and ROM was practically disabled. Instructions from RAM began executing in every clock cycle.





**Simulator Design:**

1. **ALU Circuit (Show all circuits except FA circuit)(Marks 5):**





**Check List:**

Have you added all circuits of ALU from FA to ALU Operations Circuits (ADD, XOR, SHL etc.) to Top Level ALU Circuit?	YES
--	-----

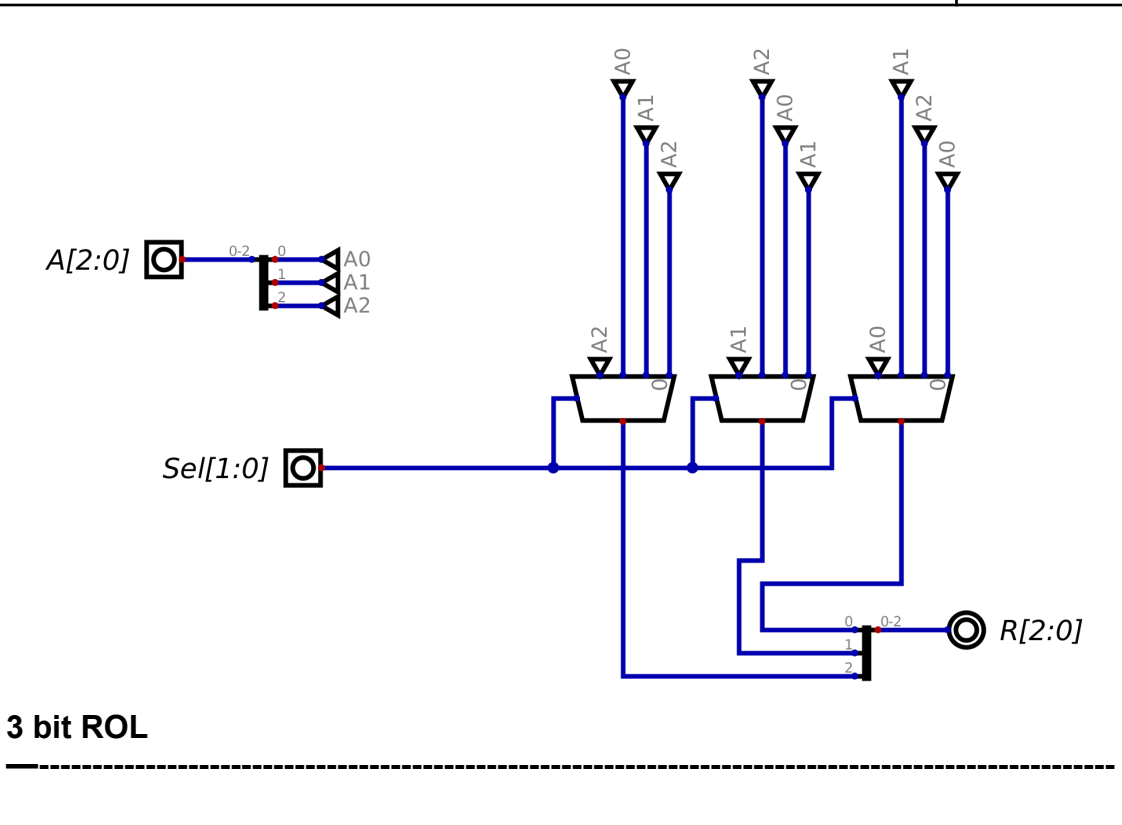


    

**3 bit OR**

    


**3 bit Adder**

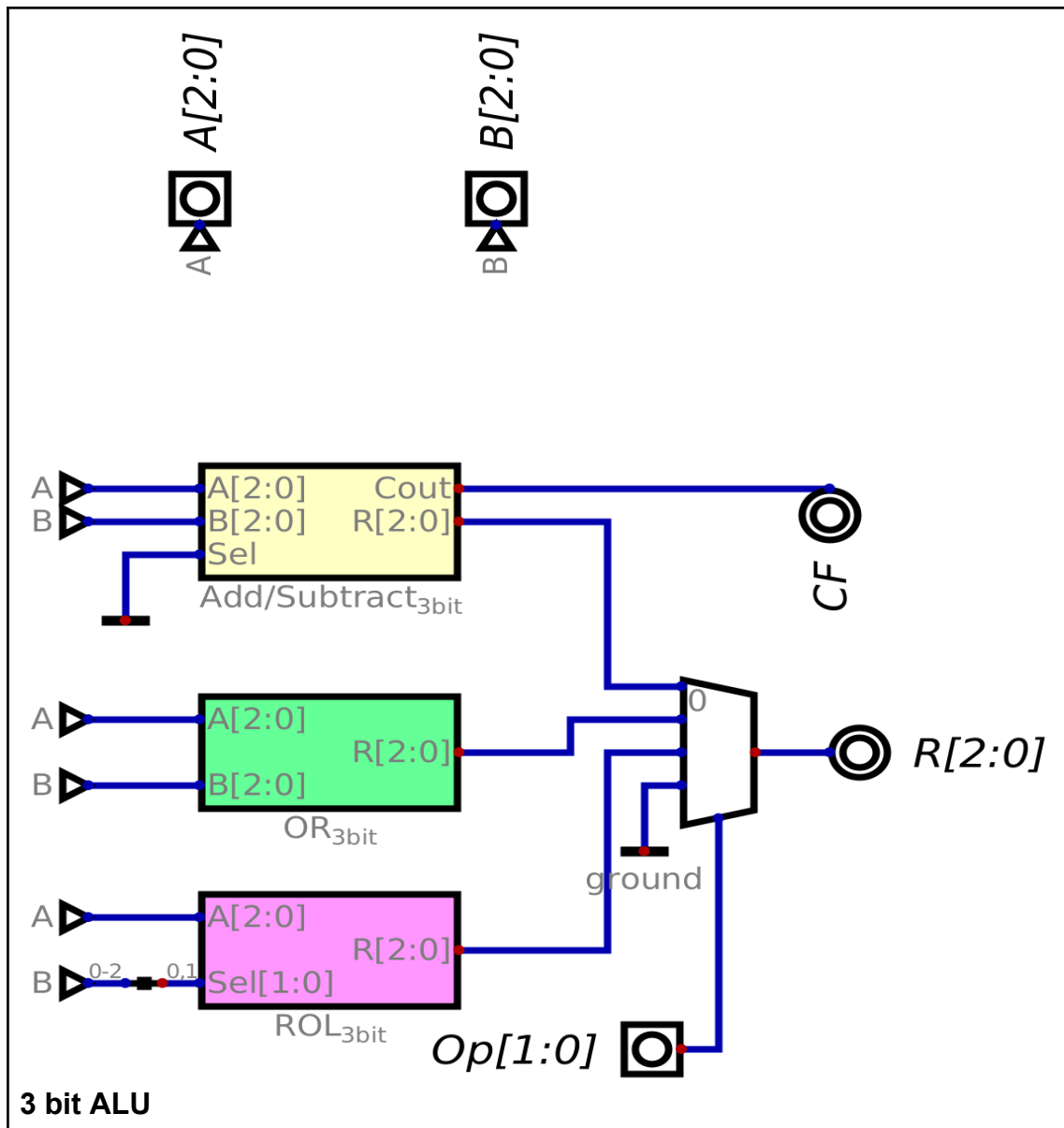


## 2. Register Set Circuit (Top to Bottom all circuits)(5 Marks):

### Check List:


Have you added all circuits of Register Set from 1 bit Register to n bit Register to Top Level Register Set Circuit.?	YES

 

**1 bit Register**

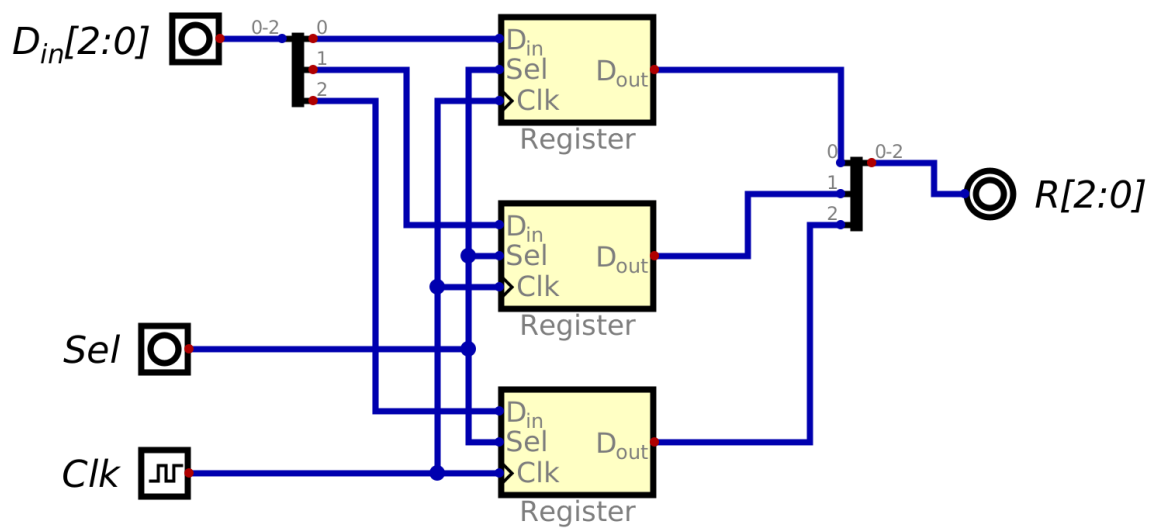


**1x3 Register**

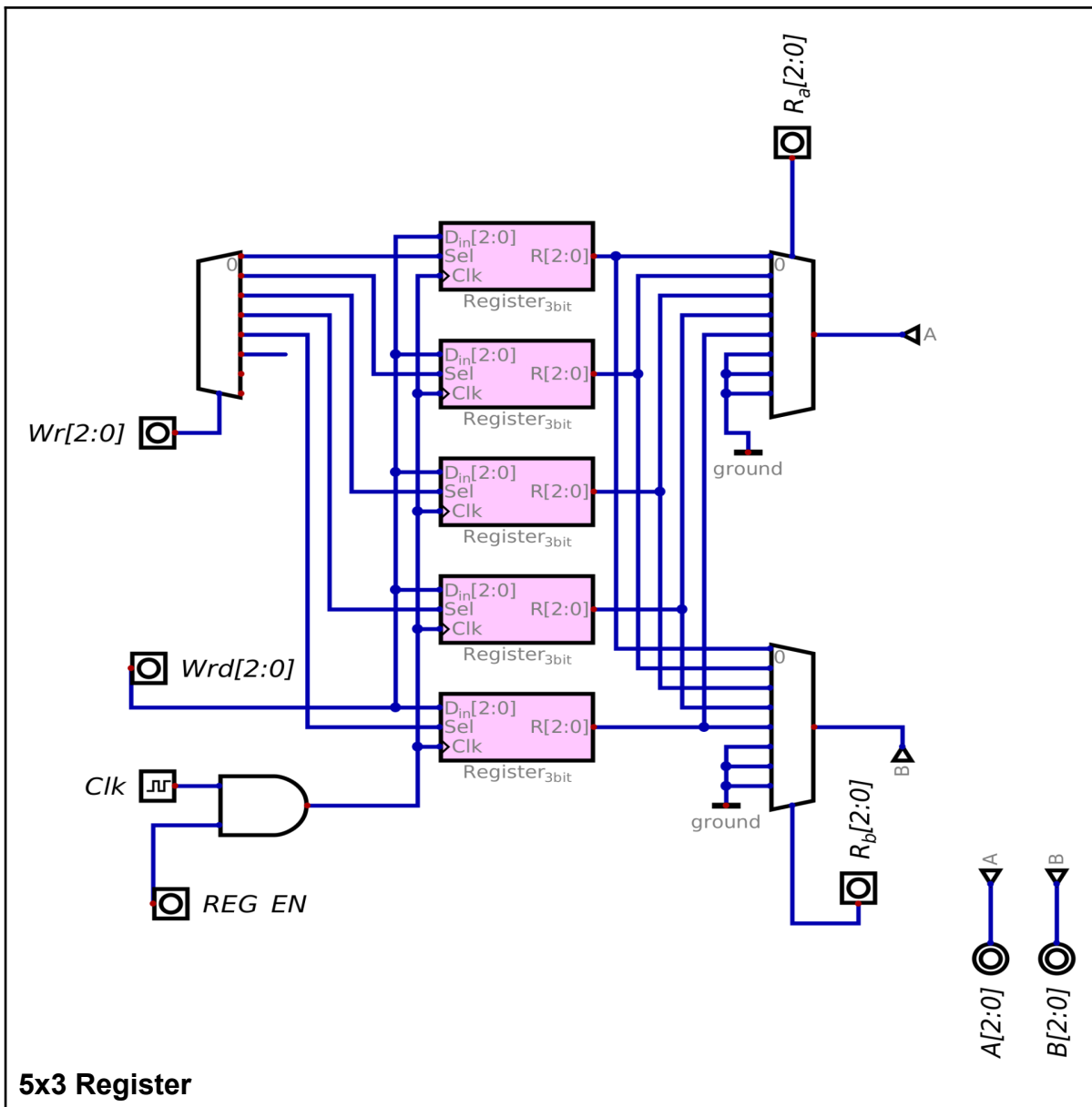



### 3. RAM Circuit (Top to Bottom all circuits)(5 Marks):

#### Check List:

Have you added all circuits of RAM from 1x1 RAM to 1xN RAM to MxN RAM?	YES
--	-----

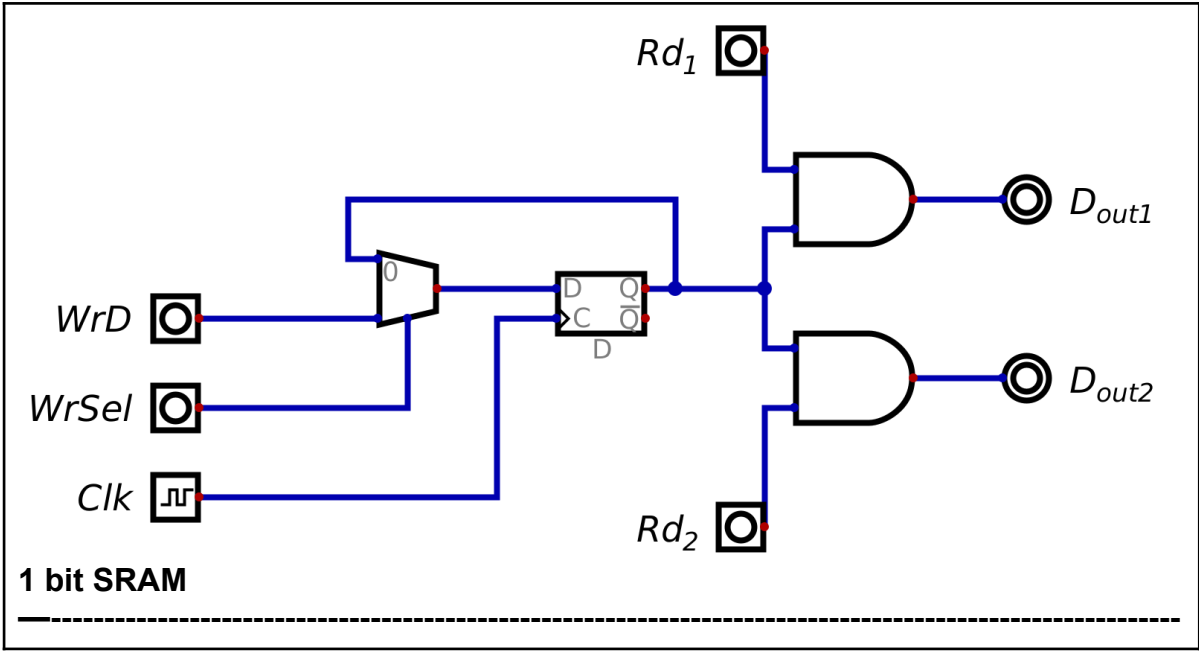

 

 

#### 4. a) ISA (2 Marks)

##### Check List:

Have you added all ISA of CPU along with its sample machine code to be run on CPU?	YES
<b>16 bit ISA with 7 addressable RAM and 5 addressable Register slots. CPU has 3 bit word size.</b>	

##### ISA (Register Mode):

Opcode (4 bit)		Register 1	Register 2	Unused
2 bits	2 bits	3 bits	3 bits	6 bit
00	00 -ADD 01 - OR 10 -ROL	Ra (000-100)	Rb (000-100)	XXXXXX

##### ISA (Immediate Mode):

Opcode (4 bit)	Register 1	Constant	Unused
----------------	------------	----------	--------



2 bits	2 bits	3 bits	3 bits	6 bit
01	00 -ADD 01 - OR 10 -ROL	Ra (000-100)	000-111	XXXXXX

**ISA (Branching Mode):**

Opcode (4 bit)		Address	Unused
2 bits	2 bits	3 bits	9 bit
10	00 -JMP 01 - JC	000-110	XXXXXXXXXX



**Sample Machine Code with assembly code in comments to be run on CPU (You will make a video running this machine code on CPU in order to prove that your CPU is working perfectly)**

Machine Code	Assembly Code
0100001101xxxxxx	ADD A1, 5
0110001001xxxxxx	ROL A1, 1
0001011001xxxxxx	OR A3, A1
0100001101xxxxxx	ADD A1, 5
1001001xxxxxxxxx	JC 1
0000011001xxxxxx	ADD A3, A1
0001011000xxxxxx	OR A3, A0
1000100xxxxxxxxx	JMP 4

**b) CPU (Top to Bottom all circuits)(3 Marks):**

**Check List:**

Have you added all circuits of CPU from Program Counter to Control Unit to Top Level CPU Circuit with <b>Output Pins showing contents of ALU, Register Set, RAM etc. (Important for CPU Verification, Check Tutorial Videos for Details)?</b>	YES
---	-----

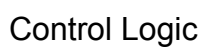 

<p>3 bit CPU</p>	
<p>Have you made a video running this sample machine code on the CPU (1 instruction at a time in a similar way shown in video) in order to prove that your CPU is working perfectly.</p> <p><a href="#">CPU Simulation Video</a></p>	<p>YES</p>